 
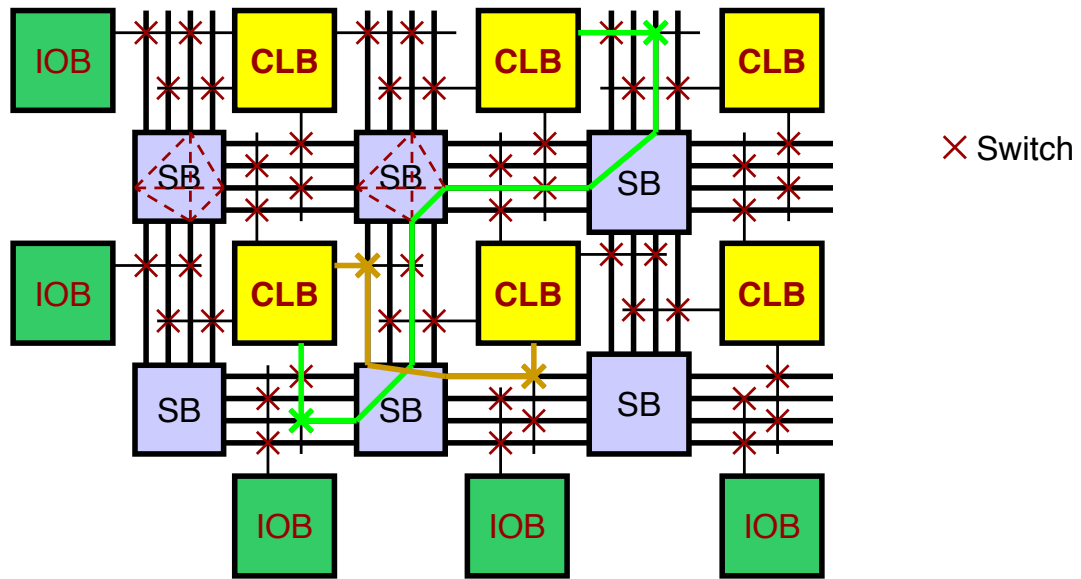

CSC 322: FPGAs and Verilog

Based on slides from John Nestor
Lafayette College
Easton, Pennsylvania 18042

FPGA Organization - Overview



FPGA Organization (Simplified)



CLB - Configurable Logic Block IOB - Input/Output Block SB - Switch Block

FPGA Tradeoffs

▶ Advantages

- ▶ Very low development cost
- ▶ Post-manufacturing changes possible
- ▶ Powerful functions in a small package
- ▶ Relatively inexpensive

▶ Disadvantages

- ▶ Inefficient - unused CLBs are still on device
- ▶ Much slower than ASICs, Custom ICs
- ▶ Higher power than ASICs, Custom ICs
- ▶ More expensive than ASICs, Custom ICs in volume

Verilog Overview

- ▶ Important Points About Verilog
- ▶ The module construct
- ▶ Combinational Logic
- ▶ Parameters
- ▶ Module Instantiation
- ▶ Sequential Logic
- ▶ Finite State Machines


Key Point: Verilog is for Hardware!

- ▶ Verilog code is ***not like software!***
 - ▶ Hardware is parallel
 - ▶ Software is sequential
- ▶ Think **hardware** and write code that describes hardware
- ▶ Follow **coding guidelines** to avoid pitfalls




Zen Master Lin Chi Yi-Sen (note stick)
source: <http://thezenfrog.wordpress.com>


Verilog Hardware Constructs

 


Combinational Logic

 

Registered Logic

 


General Sequential Logic

 

Finite State Machine (FSM)

Important Points about Verilog (cont' d)

 - ▶ Verilog is based on **event-driven simulation**
 - ▶ Signal values change at specific time points
 - ▶ Each model:
 - Activates in response to **input events**
 - Creates **output events** to represent output changes




Important Points about Verilog (cont' d)

- ▶ **Our focus: the synthesizable subset**
 - ▶ **Structural Descriptions** - module instantiations
 - ▶ **Behavioral Descriptions**
 - `assign` - continuous assignments
 - `always` blocks

Verilog module construct

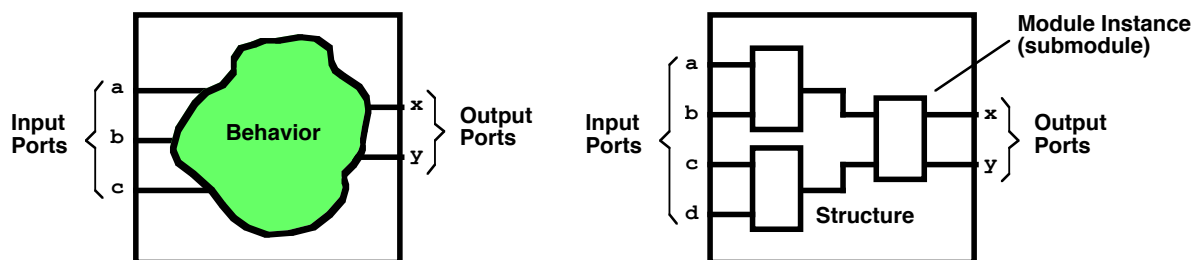- ▶ **Key building block of language**
 - ▶ **Interface** - input and output ports
 - ▶ **Body** - specifies contents of "black box"
 - behavior - what it does
 - structure - how it's built from module **instances (submodules)**
 - Mixed behavior and structure (discouraged)



First Example: Full Adder

```
module fulladder(a, b, cin, sum, cout);  
  input a, b, cin;  
  output sum, cout; } Port Declarations  
  
  assign sum = a ^ b ^ cin;  
  assign cout = a & b | a & cin | b & cin;  
endmodule
```

Ports

Semicolon


NO Semicolon

Continuous Assignment Statements (Parallel)

Comments about First Example

- ▶ **Module interface: input and output ports**
 - ▶ Single bit
 - ▶ Multiple bit - array syntax
- ▶ **Module internals:**
 - ▶ Internal connections (*wire*) and variables (*reg*)
 - ▶ Continuous assignment statements - *assign*
 - ▶ Concurrent statements - *always*
 - ▶ Submodule instantiation (hierarchy)
- ▶ **Digital values: (0, 1, X, Z)**
 - Only in simulation

Example: 7-Segment Decoder

 

```
module seven_seg(data, segments);
  input  [3:0] data;
  output [6:0] segments;

  reg [6:0] segments;

  // Output patterns:      abc_defg
  parameter BLANK = 7'b111_1111;
  parameter ZERO  = 7'b000_0001;
  parameter ONE   = 7'b100_1111;
  parameter TWO   = 7'b001_0010;
  parameter THREE = 7'b000_0110;
  parameter FOUR  = 7'b100_1100;
  parameter FIVE  = 7'b010_0100;
  parameter SIX   = 7'b010_0000;
  parameter SEVEN = 7'b000_1111;
  parameter EIGHT = 7'b000_0000;
  parameter NINE  = 7'b000_0100;
```

Port Declarations

Variable (reg) Declaration

Symbolic Constants

Example: 7-Segment Decoder Part 2

```
always @(data)
  case (data)
    4'd0: segments = ZERO;
    4'd1: segments = ONE;
    4'd2: segments = TWO;
    4'd3: segments = THREE;
    4'd4: segments = FOUR;
    4'd5: segments = FIVE;
    4'd6: segments = SIX;
    4'd7: segments = SEVEN;
    4'd8: segments = EIGHT;
    4'd9: segments = NINE;
    default: segments = BLANK;
  endcase
endmodule
```

always Statement (Parallel)

Case Statement (Sequential)

Procedural assignment statements

Verilog Overview - Language Details


- ▶ **Syntax - See Quick Reference Card**
- ▶ **Major elements of language:**
 - ▶ **Lexical Elements (“tokens” and “token separators”)**
 - Numbers
 - Identifiers
 - Operators
 - ▶ **Data Types and Values**
 - ▶ **Modules**

Lexical Elements

- ▶ **Whitespace - ignored except as token separators**
- ▶ **Comments**
 - ▶ **Single-line comments** `//`
 - ▶ **Multi-line comments** `/* ... */`
- ▶ **Numbers (special syntax to specify bit-width)**
- ▶ **Identifiers (e.g. module names, port names, etc.)**
- ▶ **Operators- unary, binary, ternary**
 - ▶ **Unary** `a = ~b;`
 - ▶ **Binary** `a = b && c;`
 - ▶ **Ternary** `a = (b < c) ? b : c;`

Numbers

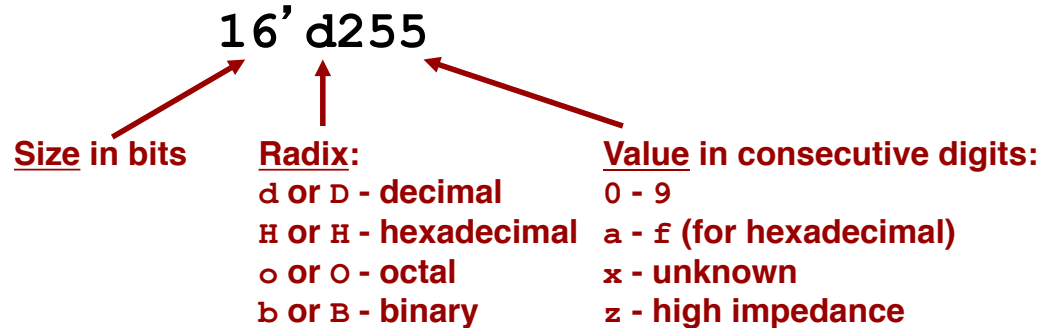- ▶ Sized numbers - with specific bitwidth and radix



4' b1101

12' h7af

12' b0111_1010_1111

Spacers

Numbers (continued)

- ▶ Unsized numbers (decimal, usually 32 bits)

0

3547

65535

- ▶ Negative numbers

-3547

-12' h3eb

-16' d1

Strings

- ▶ Character sequence in quotes (on single line)
- ▶ Treated as a sequence of 1-byte ASCII values
- ▶ Special characters - C-like (e.g., \n)

"This is a string" "a/b" "a\nb"

Identifiers

- ▶ **Standard C-like identifiers**
 - ▶ First character alphabetic or `'_'`
 - ▶ Following characters: alpha, numeric, or `'_'`
 - ▶ Identifiers are case sensitive
 - ▶ Identifiers can't be reserved words
- ▶ **"Escaped" identifiers:**
 - ▶ start with backslash
 - ▶ follow with any non-whitespace ASCII
 - ▶ end with whitespace character
- ▶ **Examples**

John paul _0george **r1ng0

Reserved Words

```
always  and      assign  begin   buf     bufif0  bufif1  case
casex   casez     cmos    deassign default defparam disable edge
else    end       endcase endfunction      endmodule
endprimitive  endspecify      endtable endtask  event   for
force   forever  fork    function highz0  highz1  if      ifnone
initial inout   input   integer join    large   macromodule
medium  module   nand    negedge nmos    nor     not
notif0  notif    or      output  parameter      pmos
posedge primitive      pull0   pull1   pulldown pullup  rcmos
real    realtime reg     release repeat  rnmos   rpmos   rtran
rtranif0 rtranif1 scalared small   specify specparam      strong0
strong1 supply0  supply1 table  task   time   tran   tranif0
tranif1 tri    tri0    tri1   triand trior  trireg vectored
wait    wand    weak0  weak1  while  wire   wor    xnor
xor
```

Data Types

- ▶ **nets** - describe “wire” connections
 - ▶ general purpose: **wire**
 - ▶ special purpose: **supply0, supply1, tri0, tri1, triand, trior, trireg, wand, wor**
- ▶ **registers** - variables
(assigned values by procedural statement)
 - ▶ **reg** - basic binary values
 - ▶ **integer** - binary word (≥32 bits - machine dependent)
 - ▶ **real** - floating point (not supported by synthesis)
 - ▶ **time** - simulation time (not supported in synthesis)
 - ▶ **realtime** - simulation time (not supported in synthesis)

More about Data Types

▶ **Vectors - Multiple-Bit Signals (net or register)**

```
wire [31:0] sum;
```


```
reg [7:0] avg;
```

▶ **Arrays - used for memories**

```
reg [7:0] mem [0:255];
```

word size

memory size

 

Logic Values

▶ **Each bit can take on 4 values:**

▶ **0** - Standard binary “FALSE”

▶ **1** - Standard binary “TRUE”

▶ **x** - UNKNOWN


▶ **z** - High Impedance

▶ **During simulation, all values are originally x**

▶ **Complication: x & z sometimes used as “wildcards” (e.g. casex, casez)**

Recap: Verilog Modules

 - ▶ **module** - key building block of language
 - ▶ **Interface** - input and output ports
 - ▶ **Body** - specifies contents of "black box"
 - behavior - what it does
 - structure - how it's built from other "black boxes"



Recap: Module Declaration

```
module modulename ( port1, port2, ... );  
    port1 direction declaration;  
    port2 direction declaration;  
    reg declarations;  
    wire declarations;  
  
    module body - "parallel" statements:  
        assign, always, initial, etc.  
  
endmodule
```

Recap: Module Example

```
module fulladder(a, b, cin, sum, cout);  
  input a, b, cin;  
  output sum, cout; } Port Declarations  
  
  assign sum = a ^ b ^ cin;  
  assign cout = a & b | a & cin | b & cin;  
endmodule
```

Ports

Port direction:
input
output
inout

Recap: Module Example - Verilog 2001


```
module fulladder(Complete Port Declarations  
  input a, input b, input cin,  
  output sum, output cout);  
  
  assign sum = a ^ b ^ cin;  
  assign cout = a & b | a & cin | b & cin;  
endmodule
```

Module Body - “Parallel” Statements

- ▶ Describe **parallel** behavior - **unlike** C/Java!
- ▶ Types of Parallel Statements:
 - ▶ **assign** - simple combinational logic with an expression
 - ▶ **always** - complex behavior for combinational or registered logic with **procedural statements**
 - ▶ module **instantiation** - used for structure
 - ▶ **initial** - used to specify startup behavior (not supported in synthesis - but **useful in simulation!**)
 - ▶ ... and other features useful only in simulation

Combinational Logic

 - ▶ Describe using Verilog “Parallel Statements”
 - ▶ Simple Expression - `assign`
 - ▶ Procedural Code - `always`



```
wire x, y;  
assign x = (a | b) & c;  
assign y = (a & b) | c;
```

```
reg x, y;  
always @(a or b or c)  
begin  
    x = (a | b) & c;  
    y = (a & b) | c;  
end
```

Continuous Assignment

▶ **General Form:**

assign *wire* = *expression*

▶ **Example:**

```
module fulladder(a, b, cin, sum, cout);  
  input a, b, cin;  
  output sum, cout;  
  
  assign sum = a ^ b ^ cin;  
  assign cout = a & b | a & cin | b & cin;  
endmodule
```

CG 3.3: Use continuous assignment for simple combinational logic.

Operators and Precedence

- ▶ Same operators as Java/C/C++ (plus a few extras)
- ▶ Override with parentheses () when needed

~	Highest
*, /, %	
+, -	
<<, >>	
<, <=, >, >=	
=, ==, !=	
&, ~&	
^, ~^	
, ~	
?:	Lowest

Bitwise Operators in Expressions

- ▶ Basic bitwise operators: identical to C/C++/Java

```
module inv(a, y);  
  input  [3:0] a; } 4-bit Ports  
  output [3:0] y;  
  
  assign y = ~a;  
endmodule
```

↑
Unary Operator: NOT

Reduction Operators in Expressions

- ▶ Apply a single logic function to multiple-bit inputs

```
module and8(a, y);  
  input  [7:0] a;  
  output          y;  
  
  assign y = &a;  
endmodule
```

↑
Reduction Operator: AND & (also supports OR |, EXOR ^)
equivalent to:
a[7] & a[6] & a[5] & a[4] & a[3] & a[2] & a[2] & a[2] & a[0]

Conditional Operators in Expressions

▶ Like C/C++/Java Conditional Operator

```
module mux2(d0, d1, s, y);
  input  [3:0] d0, d1;
  input          s;
  output [3:0] y;

  assign y = s ? d1 : d0;
  // output d1 when s=1, else d0
endmodule
```

▶ “if” statements **not allowed** in assign

Concatenation

▶ { } combines bit vectors

```
module cat(input [7:0] a, input [7:0] b,
           output [15:0] w);
```

```
  assign w = {a, b};
endmodule
```

Concatenates 8 bits + 8 bits => 16 bits

```
module adder(input [31:0] a, input [31:0] b,
             output [31:0] y, output cout);
```

```
  assign {cout, y} = a + b;
endmodule
```

32-bit add produces 33-bit result


Concatenates 1 bits + 32 bits => 33 bits

More Operators: Replication

- ▶ `{ n {pattern} }` replicates a pattern *n* times

```
module signextend(a, y);
  input  [15:0]    a;
  output [31:0]    y;

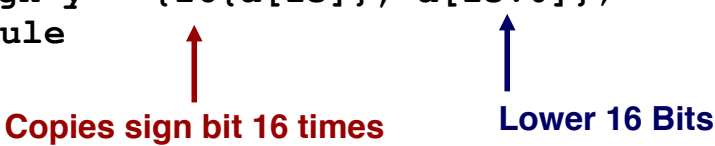  assign y = {16{a[15]}, a[15:0]};
endmodule
```



Internal Signals

- ▶ Declared using the **wire** keyword

```
module fulladder(a, b, cin, s, cout);
  input  a, b, cin;
  output s, cout;

  wire    prop;

  assign prop = a ^ b;
  assign s = prop ^ cin;
  assign cout = (a & b) | (cin & (a | b));
endmodule
```

 Important point: these statements “execute” in parallel

Combinational always blocks

▶ Motivation

- ▶ assign statements are fine for simple functions
- ▶ More complex functions require procedural modeling

▶ Basic syntax:

```
always (sensitivity-list)  
    statement ← Sequential statement (=, if/else, etc.)  
  
or  
  
always (sensitivity-list)  
begin  
    statement-sequence } Compound Statement -  
                        } sequence of sequential statements  
end
```

Combinational Modeling with always

▶ Example: 4-input mux behavioral model

```
module mux4(d0, d1, d2, d3, s, y);  
    input      d0, d1, d2, d3;  
    input [1:0] s;  
    output     y;  
    reg       y; // declare y as a variable
```

Sensitivity List (activates on change)

```
always @(d0 or d1 or d2 or d3 or s)  
    case (s)  
        2'd0 : y = d0;  
        2'd1 : y = d1;  
        2'd2 : y = d2;  
        2'd3 : y = d3;  
        default : y = 1'bx;  
    endcase  
endmodule
```

**Blocking assignments
(immediate update)**

CG 3.3 (a): Assign outputs (in comb. logic) using blocking assignment.

Verilog 2001 Sensitivity Lists

- ▶ Useful shorthand avoids common simulation errors

```
module mux4(d0, d1, d2, d3, s, y);
  input      d0, d1, d2, d3;
  input [1:0] s;
  output     y;
  reg        y;

  always @*
    case (s)
      2'd0 : y = d0;
      2'd1 : y = d1;
      2'd2 : y = d2;
      2'd3 : y = d3;
      default : y = 1'bx;
    endcase
endmodule
```


Activates on any input change
d0, d1, d2, d3

CG 3.3 (e): Use the Verilog 2001 construct `always @*` when supported.

Modeling with Hierarchy

- ▶ Create instances of submodules
- ▶ Example: Create a 4-input Mux using `mux2` module
- ▶ Original `mux2` module:
 
```
module mux2(d0, d1, s, y);
  input [3:0] d0, d1;
  input      s;
  output [3:0] y;
  assign y = s ? d1 : d0;
endmodule
```



Module Instantiation (Positional)

- ▶ Create instances of submodules
- ▶ Example: Create a 4-input Mux using `mux2` module

```
module mux4(d0, d1, d2, d3, s, y);
  input  [3:0] d0, d1, d2, d3;
  input  [1:0] s;
  output [3:0] y;

  wire   [3:0] low, high;

  mux2 U_LOW(d0, d1, s[0], low);
  mux2 U_HIGH(d2, d3, s[0], high);
  mux2 U_FINAL(low, high, s[1], y);
endmodule
```

↑ Instance Names ↑ Connections (Positional)

Module Instantiation (Explicit)

- ▶ Preferable for long port lists

```
module mux4(d0, d1, d2, d3, s, y);
  input  [3:0] d0, d1, d2, d3;
  input  [1:0] s;
  output [3:0] y;

  wire   [3:0] low, high;

  mux2 U_LOW(.d0(d0), .d1(d1), .s(s[0]), .y(low));
  mux2 U_HIGH(.d0(d2), .d1(d3), .s(s[0]), .y(high));
  mux2 U_FINAL(.d0(low), .d1(high), .s(s[1]), .y(y));
endmodule
```

CG 2.4: Use the explicit connection style when instantiating modules with more than 3 ports.

Parameterized Modules

▶ Parameters - define values that can change

▶ Declaration:

```
module mod1(in1, in2, out1, out2);  
    parameter N=default-value; ← Defines Parameter N  
    input  [N-1 : 0] in1, in2;  
    output [N-1 : 0] out1;  
    ...  
endmodule ← Uses Parameter N
```

▶ Instantiation:

```
wire [7:0] w, x, y; ← Sizes must match  
wire z; ← instantiated value!  
mod1 #(8) U_MOD1(w,x,y,z);  
      ↑  
      Sets Parameter N for instance U_MOD1
```

Parameterized Modules: Example

▶ N-bit 2-1 multiplexer (parameterized bitwidth)

```
module mux2( sel, a, b, y );  
    parameter bitwidth=32; ← Defines Parameter bitwidth  
    input      sel; ← (default value:32)  
    input  [bitwidth-1:0] a, b;  
    output [bitwidth-1:0] y;  
    assign y = sel ? b : a;  
endmodule ← Uses Parameter bitwidth  
           to set input, output size
```

▶ Instantiations

```
mux2 #(16) U_MUX_26(s, a, b, c); ← 16-bit mux  
mux2 #(5)  U_MUX_5(s, d, e, f); ← 5-bit mux  
mux2 #(32) U_MUX_32(s, g, h, i); ← 32-bit mux  
mux2 U_MUX_32D(s, j, k, l); ← 32-bit mux (default)
```

Symbolic Constants with Parameters

- ▶ **Idea: use parameter to name “special constants”**

```
parameter RED_ALERT = 2'b11;  
parameter YELLOW_ALERT = 2'b01;  
parameter GREEN_ALERT = 2'b00;
```

- ▶ **Don't change in module instances**
- ▶ **Do this to make your code more understandable**
 - ▶ For others reading your code
 - ▶ For yourself reading your code after some time has passed

CG 1.9: Use symbolic constants in your code instead of “magic numbers”.
Use the `parameter` construct for local constants.

Symbolic Constants using ``define`

- ▶ Like C/C++, Verilog has a preprocessor
- ▶ ``define` - equivalent to `#define` in C/C++
- ▶ **Symbolic constant definition:**

```
`define ZERO 7'b0000_000
```

- ▶ **Symbolic constant usage: preface with “`”**

```
segments = `ZERO;
```

- ▶ **Other preprocessor directives**

- ▶ ``ifdef`
- ▶ ``else`
- ▶ ``endif`

Used for **conditional compilation**

CG 1.9 Use the ``define` compiler directive for global constants
(parameters are local to a module).

Sequential Design in Verilog - Basic Constructs


Describe edge-triggered behavior using:

- ▶ always block with "edge event"
 - ▶ `always @(posedge clock-signal)` ← for positive edge-trigger
 - ▶ `always @(negedge clock-signal)` ← for negative edge-trigger

▶ Nonblocking assignments (<=)


```
@always (posedge clock-signal)
begin
    output1 <= expression1;
    . . .
    output2 <= expression2;
    . . .
end
```

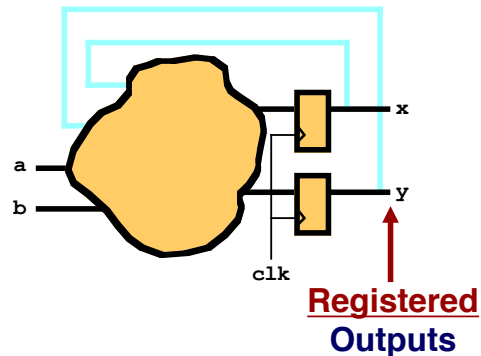Non-Blocking Assignments
(deferred update)




Simple Examples: Flip-Flop, Register
 
```
module flipflop(d, clk, q);
    input    d;
    input    clk;
    output   q;
    reg     q;
    always @(posedge clk)
        q <= d;
endmodule
```


 
```
module flop3(clk, d, q);
    input    clk;
    input    [3:0] d;
    output   [3:0] q;
    reg     [3:0] q;
    always @(posedge clk)
        q <= d;
endmodule
```




Simple Example: Register with Reset

▶ Synchronous - resets on clock edge if reset=1

```
module flopr(clk, reset, d, q);
  input      clk;
  input      reset;
  input [3:0] d;
  output [3:0] q;

  reg [3:0] q;

   always @(posedge clk)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule
```




Simple Example: Register with Reset

▶ Asynchronous - resets immediately if reset=1

```
module flopr(clk, reset, d, q);
  input      clk;
  input      reset;
  input [3:0] d;
  output [3:0] q;

  reg [3:0] q;

  always @(posedge clk or posedge reset)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule
```

 

CG 4.3: Use asynchronous reset only for system reset and initialization.

Another Example: Shift Register

```
module shiftreg(clk, sin, q);
    input      clk;
    input      sin;
    output [3:0] q;

    reg        [3:0] q;

    always @(posedge clk)
    begin
        q[0] <= sin;
        q[1] <= q[0];
        q[2] <= q[1];
        q[3] <= q[2];
    end
endmodule
```

CG 4.2: Assign (registered) outputs using nonblocking (<=) assignment.

Blocking Assignments with Reg. Outputs

```
module not_a_shiftreg(clk, sin, q);
    input      clk;
    input      sin;
    output [3:0] q;

    reg        [3:0] q;

    always @(posedge clk)
    begin
        q[0] = sin;
        q[1] = q[0];
        q[2] = q[1];
        q[3] = q[2];
    end
endmodule
```

CG 4.2: Assign (registered) outputs using nonblocking (<=) assignment.

Shift Register Application

```
module debounce (pb, clk_100Hz, pb_debounced);
  input    pb;
  input    clk_100Hz;
  output   pb_debounced;
  reg      pb_debounced;

  reg [3:0] shift_pb;

  always @ (posedge clk_100Hz) begin
    shift_pb [3:0] <= {shift_pb [2:0], pb};
    if (shift_pb == 4'b1111) pb_debounced <= 1;
    else pb_debounced <= 0;
  end
endmodule // debounce
```

What does this circuit do?
How does it work?

Another Example: 4-bit Counter

▶ Basic Circuit:

```
module counter(clk, Q);
  input clk;
  output [3:0] Q;
  reg [3:0] Q; // Q assigned a value in always


  always @(posedge clk)
  begin
    Q <= Q + 1;
    carry <= Q == 4'b1111; // WRONG!
  end
endmodule
```

▶ Questions: How about carry?

- ▶ Putting carry in this code would “register” carry
- ▶ Result: carry delayed one clock cycle
- ▶ Need to **mix** sequential & combinational logic

General Sequential Circuits

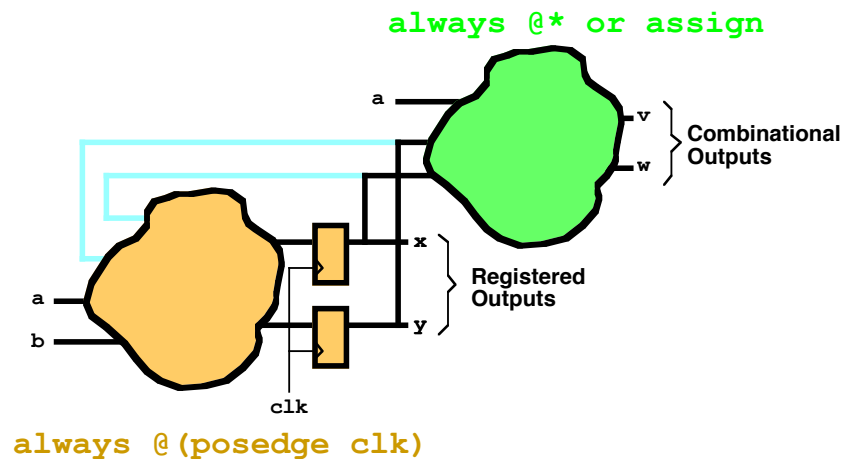- ▶ General circuit - both registered and comb. outputs
- ▶ Approach: multiple `always` blocks



Example: Adding carry to 4-bit Counter

```
module counter(clk, Q, carry);
  input clk;
  output [3:0] Q;
  output carry;

  reg [3:0] Q; // Q assigned a value in always

  assign carry = (Q == 4'b1111); } Combinational Output

  always @(posedge clk)
  begin
    Q <= Q + 1;
  end } Registered Output
endmodule
```

Refining the Counter: Synchronous Reset

```
module counter(clk, clr, Q, carry);
    input clk, clr;
    output [3:0] Q;
    output carry;

    reg [3:0] Q; // Q assigned a value in always

    assign carry = (Q == 4'b1111);

    always @( posedge clk )
    begin
        if (clr) Q <= 4'd0;
        else Q <= Q + 1;
    end
endmodule
```

} Q changes on clk edge
(usually preferred)

Refining the Counter: BCD Counter

```
module bcdcounter(clk, reset, enb, Q, carry);
    input clk, reset, enb;
    output [3:0] Q;
    output carry;

    reg [3:0] Q; // a signal that is assigned a value

    assign carry = (Q == 9) & enb;

    always @( posedge clk )
    begin
        if (reset) Q <= 0;
        else if (enb)
            begin
                if (carry) Q <= 0;
                else Q <= Q + 1;
            end
        end
    end
endmodule
```



Q: How could we make a parameterized counter?

State Machine Design

- ▶ **Traditional Approach:**
 - ▶ Create State Diagram
 - ▶ Create State Transition Table
 - ▶ Assign State Codes
 - ▶ Write Excitation Equations & Minimize
- ▶ **HDL-Based State Machine Design**
 - ▶ Create State Diagram (optional)
 - ▶ Write HDL description of state machine
 - ▶ Synthesize

Review - State Transition Diagrams

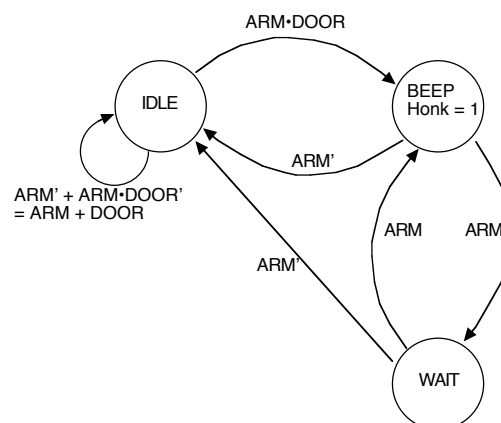 
- ▶ "Bubbles" - states
- ▶ Arrows - transition edges labeled with condition expressions
- ▶ **Example: Car Alarm**



Review - State Transition Table


▶ Transition List - lists edges in STD

PS	Condition	NS	Output
IDLE	ARM' + DOOR'	IDLE	0
IDLE	ARM*DOOR	BEEP	0
BEEP	ARM	WAIT	1
BEEP	ARM'	IDLE	1
WAIT	ARM	BEEP	0
WAIT	ARM'	IDLE	0

 

Coding FSMs in Verilog - Standard Form

- ▶ Clocked `always` block - state register
- ▶ Combinational `always` block -
 - ▶ next state logic
 - ▶ output logic

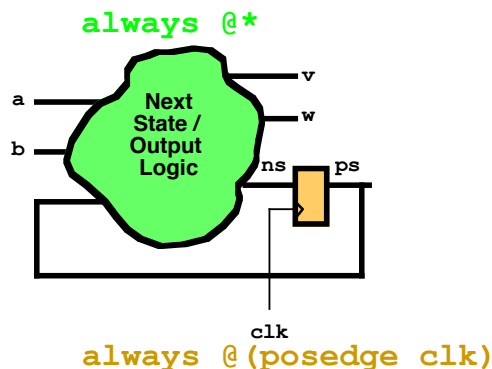

CG 5.1: Use separate `always` blocks for sequential (state register) and combinational parts of the FSM.

Coding FSMs in Verilog - Code Skeleton

▶ Part 1 - Declarations

```
module fsm(inputs, outputs);
    input . . . ;
    input . . . ;
    reg . . . ;

    parameter [NBITS-1:0]
        S0 = 2'b00;
        S1 = 2'b01;
        S2 = 2b'10;
        S3 = 2b'11;
    reg [NBITS-1 :0] CURRENT_STATE;
    reg [NBITS-1 :0] NEXT_STATE;
```

} State Codes

} State Variable

CG 5.3: Define state codes as symbolic constants using `parameter`.

Coding FSMs in Verilog - Code Skeleton

▶ Part 2 - State Register, Logic Specification

```
always @(posedge clk)
begin
    if (reset) CURRENT_STATE <= S0;
    else CURRENT_STATE <= NEXT_STATE;
end

always @(CURRENT_STATE or xin)
begin
    . . . Assign default output values
    case (CURRENT_STATE)
        S0: . . . determine NEXT_STATE, outputs
        S1 : . . . determine NEXT_STATE, outputs
        . . .
        default: . . . set NEXT_STATE, outputs for error
    end case
end // always
endmodule
```

FSM Example - Car Alarm

► Part 1 - Declarations, State Register

```
module car_alarm (arm, door, reset, clk, honk );  
  input arm, door, reset, clk;  
  output honk;  
  reg honk;
```


```
parameter IDLE=0,BEEP=1,HWAIT=2;  
reg [1:0] current_state, next_state;
```

```
always @(posedge clk)  
  if (reset) current_state <= IDLE;  
  else current_state <= next_state;
```

FSM Example - Car Alarm

► Part 2 - Logic Specification

```
always @(current_state or arm or door)  
  begin  
    honk = 0; // default value  
    case (current_state)  
      IDLE :  
        begin  
          honk = 0;  
          if (arm && door) next_state = BEEP;  
          else next_state = IDLE;  
        end  
      BEEP:  
        begin  
          honk = 1;  
          if (arm) next_state = HWAIT;  
          else next_state = IDLE;  
        end  
    end  
  end
```

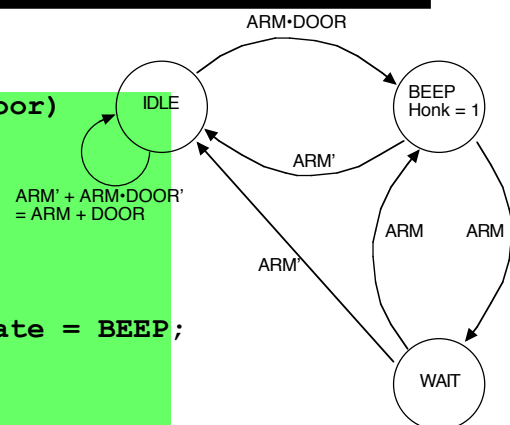


FSM Example - Car Alarm

▶ Part 3 - Logic Specification (cont' d)

```


HWAIT :
  begin
    honk = 0;
    if (arm) next_state = BEEP;
    else next_state = IDLE;
  end
default :
  begin
    honk = 0;
    next_state = IDLE;
  end
endcase
end
endmodule

```

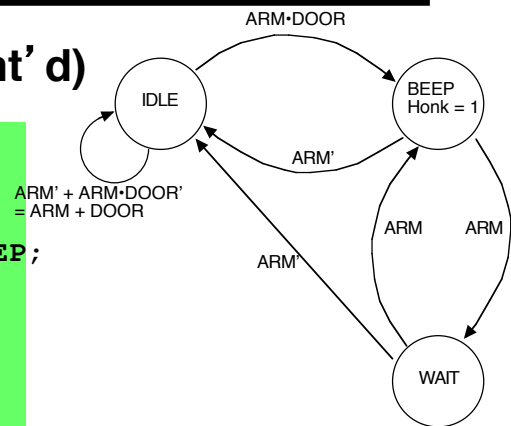


Coding FSMs in Verilog - Alternate Form

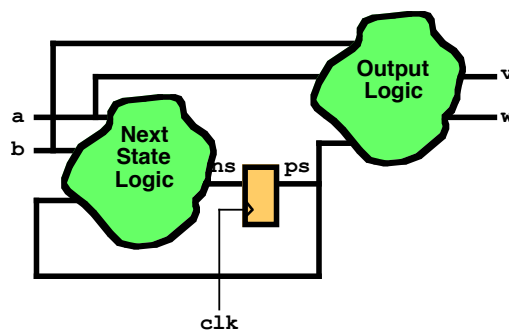- ▶ Clocked always block - state register
- ▶ Two separate combinational blocks
 - ▶ next state logic (always)
 - ▶ output logic (always or assign)



FSM Example - Verilog Handout

▶ Divide-by-Three Counter

 

Divide by Three Counter - Part 1

```
module divideby3FSM(clk, reset, out);
  input          clk;
  input          reset;
  output         out;

  reg            [1:0] state;
  reg            [1:0] nextstate;

  parameter      S0 = 2'b00;
  parameter      S1 = 2'b01;
  parameter      S2 = 2'b10;

  // State Register

  always @(posedge clk)
    if (reset) state <= S0;
    else       state <= nextstate;
```

Divide by Three Counter - Part 2


```
// Next State Logic

always @(state)
  case (state)
    S0: nextstate = S1;
    S1: nextstate = S2;
    S2: nextstate = S0;
    default: nextstate = S0;
  endcase


// Output Logic

assign out = (state == S2);
endmodule
```

Larger Example: MIPS Control Unit

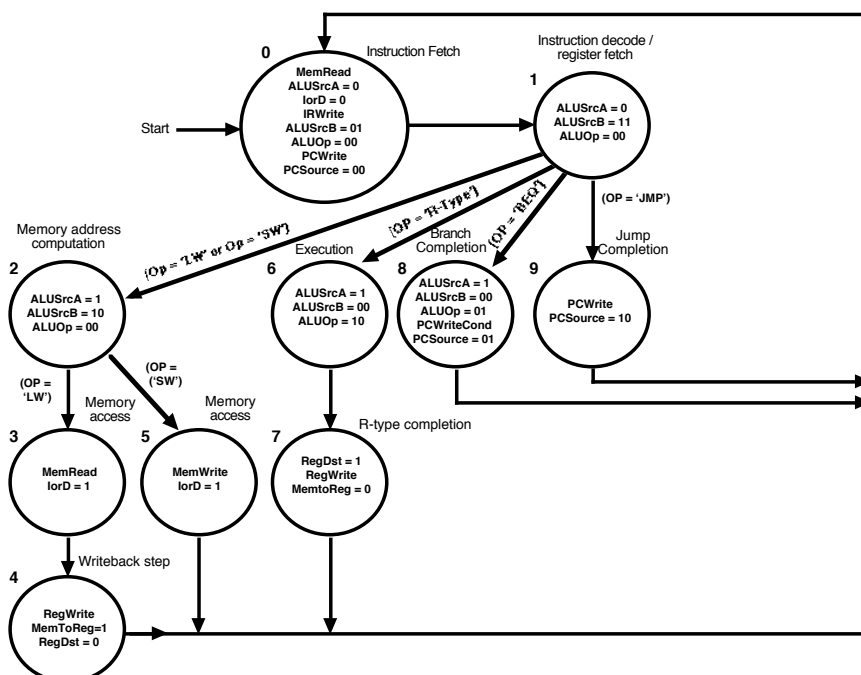

Review: Full Multicycle Implementation

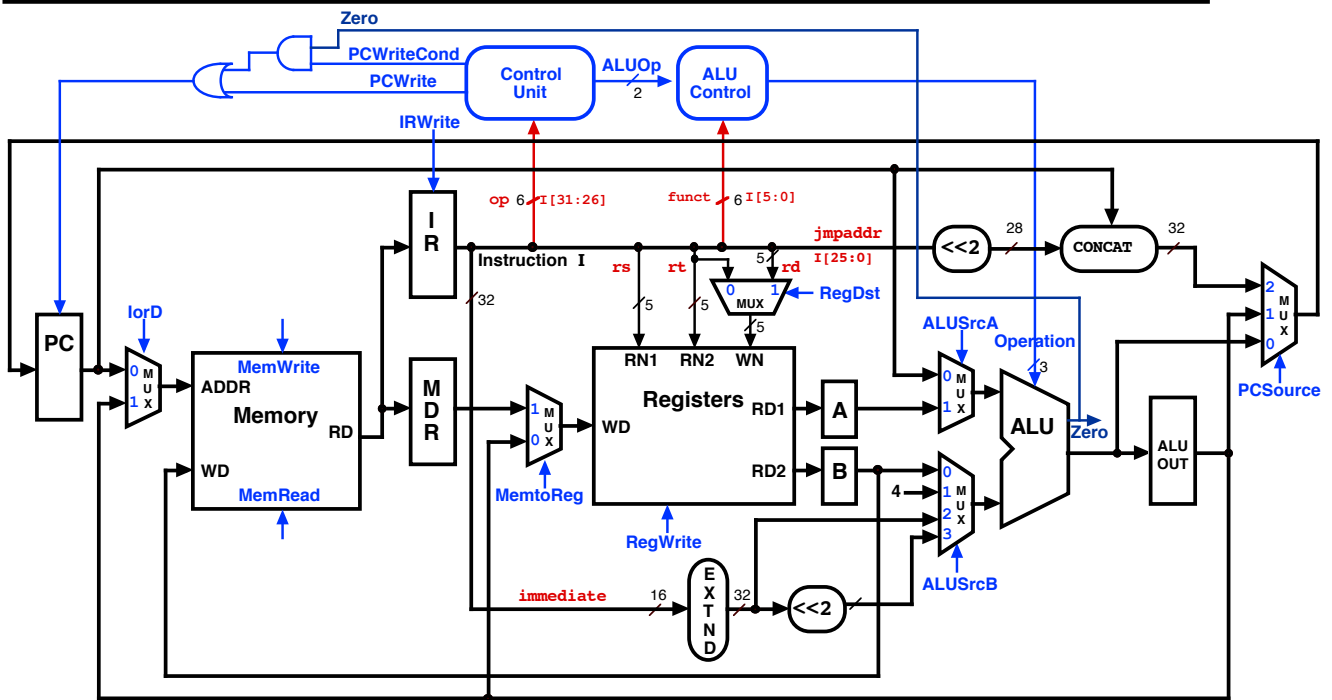

CSC322 Fall 2015

Computer Organization Lab

75

MIPS Control Unit "Skeleton" - Part 1

```
module mips_control( clk, reset, Op, PCWrite, PCWriteCond, IorD, MemRead,
    MemWrite, MemtoReg, IRWrite, PCSource, ALUOp
    ALUSrcB, ALUSrcA, RegWrite, RegDst );
```

```
input clk;
input reset;
input [5:0] Op;
output PCWrite;
output PCWriteCond;
output IorD;
output MemRead;
output MemWrite;
output MemtoReg;
output IRWrite;
output [1:0] PCSource;
output [1:0] ALUOp;
output ALUSrcA;
output [1:0] ALUSrcB;
output RegWrite;
output RegDst;
```

port declarations

CSC322 Fall 2015

Computer Organization Lab

76

MIPS Control Unit “Skeleton” - Part 2

```

reg PCWrite;
reg PCWriteCond;
reg IorD;
reg MemRead;
reg MemWrite;
reg MemtoReg;
reg IRWrite;
reg [1:0] PCSource;
reg [1:0] ALUOp;
reg ALUSrcA;
reg [1:0] ALUSrcB;
reg RegWrite;
reg RegDst;

```

reg declarations for output ports

```

parameter R_FORMAT = 6'd0;
parameter LW       = 6'd35;
parameter SW       = 6'd43;
parameter BEQ      = 6'd4;
parameter J        = 6'd2;

```

Symbolic Constants -
opcodes

```

parameter S0=4'd0, S1=4'd1, S2=4'd2, S3=4'd3, S4=4'd4,
           S5=4'd5, S6=4'd6, S7=4'd7, S8=4'd8, S9=4'd9;

```

Symbolic Constants -
state codes

MIPS Control Unit - Part 3

```

reg [3:0] current_state, next_state;

always @(negedge clk)
begin
  if (reset) current_state <= S0;
  else current_state <= next_state;
end

always @(current_state or Op)
begin
  // default values
  PCWrite = 1'b0;
  PCWriteCond = 1'b0;
  IorD     = 1'bx;
  MemRead  = 1'b0;
  MemWrite = 1'b0;
  MemtoReg = 1'bx;
  IRWrite  = 1'b0;
  PCSource = 2'bxx;
  ALUOp    = 2'bxx;
  ALUSrcA  = 1'bx;
  ALUSrcB  = 2'bxx;

```

Default
Values

```

RegWrite = 1'b0;
RegDst   = 1'bx;

```

More Default
Values

```

case (current_state)
S0: begin
  MemRead = 1'b1;
  ALUSrcA = 1'b0;
  IorD    = 1'b0;
  IRWrite = 1'b1;
  ALUSrcB = 2'b01;
  ALUOp   = 2'b00;
  PCWrite = 1'b1;
  PCSource = 2'b00;
  next_state = S1;
end
...
endcase
end

endmodule


```

State S0


(More states here)

FPGA CAD Tool Flow

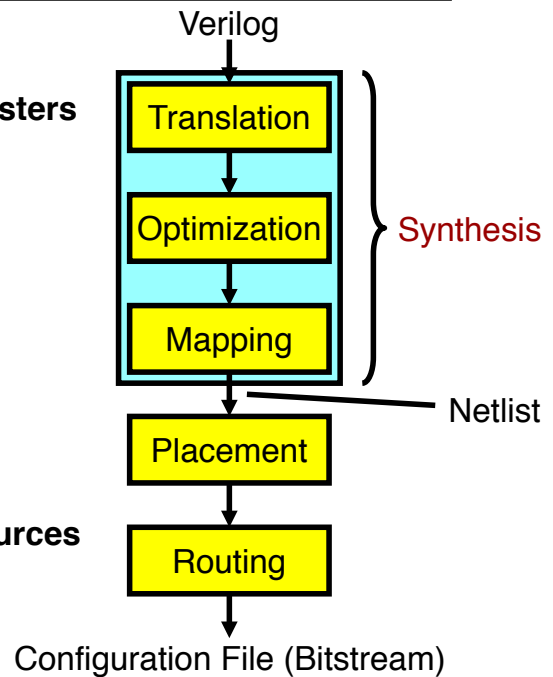- ▶ **Synthesis**
 - ▶ Translates Verilog into logic and registers
 - ▶ Optimizes logic to reduce cost and maximize speed
 - ▶ Maps logic into lookup tables (LUTs)
- ▶ **Placement**
 - ▶ Assigns LUTs to physical locations
 - ▶ Attempts to ensure routability and performance
- ▶ **Routing**
 - ▶ Assigns connections to routing resources
 - ▶ Fixes configuration of interconnect switches



Review: Modeling Logic with always

 


Combinational Logic

```
reg x, y;
always @(a or b or c)
begin
  x = (a | b) & c;
  y = (a & b) | c;
end
```

Sequential Statements

Blocking Assignments
(immediate update)

 

Registered Logic

```
reg x, y;
always @(posedge clk)
begin
  x <= a & ~x;
  y <= b & ~y;
end
```

Sequential Statements

Non-Blocking Assignments
(deferred update)


Sequential Statements

- ▶ **Assignment**
 - ▶ **Blocking assignment (=)** - for combinational logic
 - ▶ **Non-Blocking assignment (<=)** - for registered logic
- ▶ **if / else**
- ▶ **case, casez, and casex**
- ▶ **for**
- ▶ **repeat (*expr*)**

Sequential Statements We Won't Use

- ▶ **forever**
- ▶ **wait**
- ▶ **fork, join, disable**
- ▶ **assign (inside an always block)**
- ▶ **deassign**


```
always @*  
begin  
    y = 0;  
    if (a==b) assign y = v + w;  
end
```



Synthesizing if/else

▶ if/else statements create **multiplexers**
 
```
always @(c or d or x or y) begin
  if (c == 1'b1) z = x + y;
  else z = x - y;
  if (d == 1'b0) w = z;
  else w = x;
end
```



Synthesizing if/else/if

▶ if/else/if statements create **priority encoder**

```
module priority (sel, code);
  input  [7:0] sel;
  output [2:0] code;
  reg      code;


  always @(sel)
  begin
    if (sel[0]) code = "000";
    else if (sel[1]) code = "001";
    else if (sel[2]) code = "010";
    else if (sel[3]) code = "011";
    else if (sel[4]) code = "100";
    else if (sel[5]) code = "101";
    else if (sel[6]) code = "110";
    else if (sel[7]) code = "111";
    else
      code = 3'bxxx;
  end
endmodule
```

Warning: long delays!

Synthesizing if without else

- ▶ if without else: output depends on previous value

 
```
always @(a or x or y)
begin
    w = 0;
    . . .
    if (a == 1'b1) w = x + y;
end
```




Latch Inference in if without else

- ▶ What if no previous value is specified?
 - ▶ Must preserve the semantics of the language:
“reg” acts like a variable which must be stored
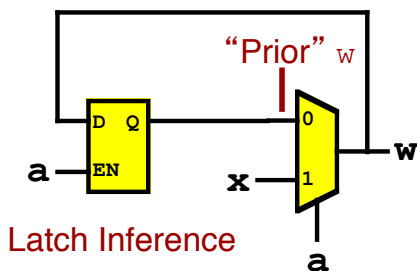
```
always @(a or x) begin
    if (a == 1'b1) w = x;
end
```



Latch Inference

 

Optimized Latch Inference

CG 4.1: Use flip-flops for sequential logic. Never use latches.

The case statement

- ▶ Similar to C/Java switch with break built in
- ▶ Simulator treats case like if / else if / else ...

```
case (e)
  2'b00 : w = x + y;
  2'b01 : w = x - y;
  2'b10 : w = x & y;
  default: w = 4'b0000;
endcase
```


==

```
if (e == 2'b00) w = x + y;
else if (e == 2'b01) w = x - y;
else if (e == 2'b10) w = x & y;
else w = 4'b00;
```


Synthesizing case

- ▶ Converts case to multiplexer (“parallel” case)
- ▶ Specify outputs for all cases (“full case”) or latch inferences occur.
 
```
case (e)
  2'd0 : w = x;
  2'd1 : w = y;
  2'd2 : w = x + y;
  default: w = 4'b0000;
endcase
```


 
```
case (e)
  2'd0 : w = xy;
  2'd1 : w = y;
  2'd2 : w = x + y;
  // 2'b11 not covered!
endcase
```




The casez and casex statements

- ▶ **casez** - allows '?' or 'z' as "wild card" digits (? preferred)
- ▶ **Casex** - allows 'x' as "wild card" digits (discouraged)

```
casez (e)
  2'b00 : w = x + y;
  2'b01 : w = x - y;
  2'b1? : w = x & y;
endcase
```

==

```
casex (e)
  2'b00 : w = x + y;
  2'b01 : w = x - y;
  2'b1x : w = x & y;
endcase
```

 


CG 3.7: Use *casez* to specify case values with wild card digits. Express wild card digits using '?' instead of 'z'. Do not use the *casex* statement.


Synthesizing casez

- ▶ **Parallel case** (select input matches one & only one case) - synthesizes to multiplexer
- ▶ **Non-parallel case** - synthesizes to priority encoder
 
```
casez (e)
  2'b00 : w = x;
  2'b01 : w = y;
  2'b1? : w = x + y;
endcase
```



 
```
begin
  w = 2'd0;
  casez (x)
    3'b1?? : w = 2'd3;
    3'b?1? : w = 2'd2;
    3'b??1 : w = 2'd1;
  endcase
end
```



Synthesis Directives for case

- ▶ **ISE (and other tools) allow directives in comments**
 - ▶ `parallel case` - force case to be treated as parallel (even if it isn't)
 - ▶ `full_case` - force case to be treated as full (even if it isn't)
- ▶ **Problems - mismatch between HW & simulation (don't use!)**
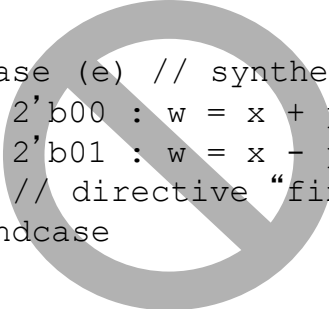
```
case (e) // synthesis full_case
  2'b00 : w = x + y;
  2'b01 : w = x - y;
  // directive "fixes" missing default
endcase
```



Loops: for and repeat

- ▶ `for(i=0; i<=n; i=i+1) statement`
 - ▶ Identical to C/Java
 - ▶ Supported in synthesis with constant start/finish (e.g., 0, 9) - loop unrolled
 - ▶ Supported in simulation for all values
- ▶ `repeat(n) statement`
 - ▶ Repeats statement n times
 - ▶ Supported in synthesis with constant n - loop unrolled
 - ▶ Supported in simulation for all values

The Sensitivity List Pitfall

- ▶ You must include all inputs in sensitivity list for comb. logic
- ▶ OR... mismatch between synthesis & simulation!
- ▶ Quick fix: use @* instead (if supported)

Missing: or y
↓

```
always @(e or x) begin
  case (e)
    2'b00 : w = x + y;
    2'b01 : w = x - y;
    2'b10 : w = x & y;
    default: w = 4'b0000;
  endcase
end
```

Implies all inputs
↓


```
always @* begin
  case (e)
    2'b00 : w = x + y;
    2'b01 : w = x - y;
    2'b10 : w = x & y;
    default: w = 4'b0000;
  endcase
end
```

CG 3.3 (e): Use the Verilog 2001 construct `always @*` when supported.

Verilog Primitives


- ▶ Built-in modules for basic logic functions
- ▶ Instantiated like modules; first port always output
- ▶ Convenient to describe “glue logic”
 
```
module mux2s(d0, d1, s, y);
  wire sbar, y0, y1;
  not INV1(sbar, s);
  and AND1(y0, d0, sbar);
  and AND2(y1, d1, s);
  or OR1(y, y0, y1);
endmodule;
```




Tri-State Outputs

 - ▶ **Used in interfaces**
 - ▶ Allows a module to “electrically disconnect” by placing output in a high-impedance “z” state
 - ▶ Allows connected devices to share wires
- ▶ **Example: Processor/Peripheral Bus Interface**
 - ▶ Processor Write - Processor drives bus, peripheral reads
 - ▶ Processor Read - Peripheral drives bus, processor reads




Tri-State Outputs in Verilog

Write Your Own

 


```
module tbuf(w, en, y);  
  input w, en;  
  output y;  
  
  assign y = en ? w : 1'bz;  
endmodule
```

Or Use Primitives:

 


```
bufif1(y, x, en)
```

 

```
bufif0(y, w, en_n)
```




Complex Logic in Verilog

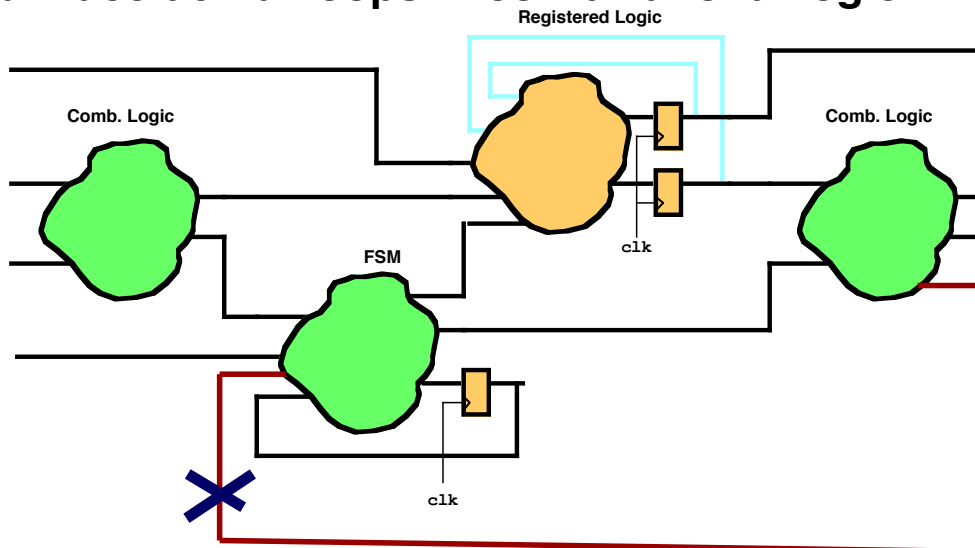  - ▶ Create by combining basic building blocks
- ▶ Pitfall: accidental loops in combinational logic




Review - Flip-Flop Timing

- ▶ Propagation Delay t_{CQ}
- ▶ Setup time t_{setup}
- ▶ Hold time t_h



FPGA Timing Analysis

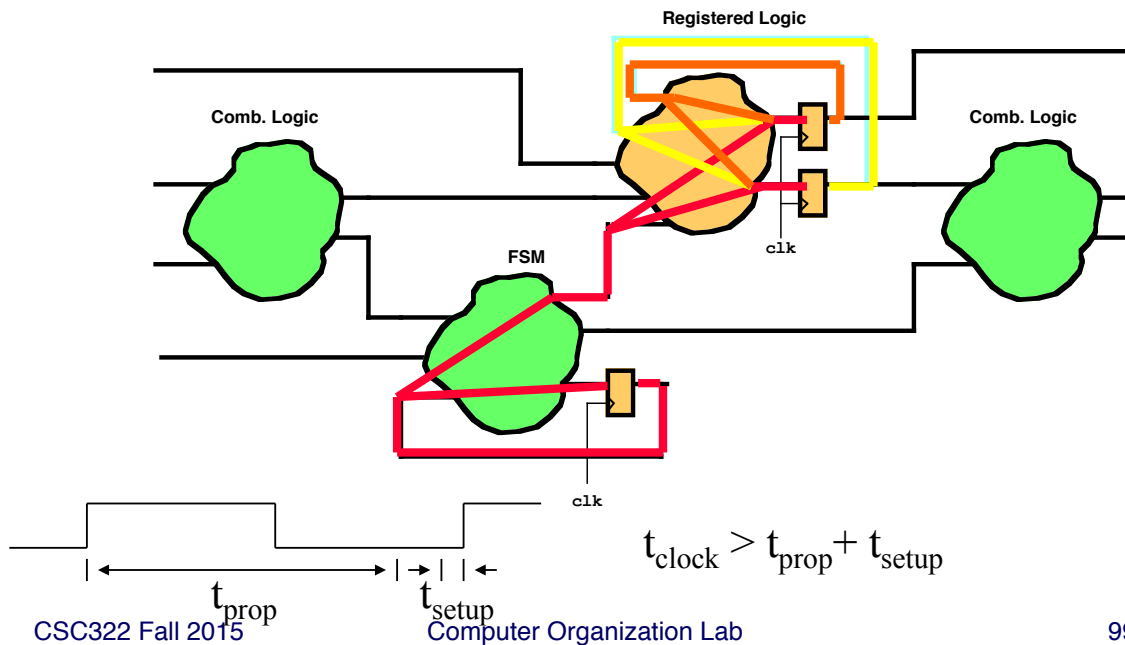- ▶ Timing analyzer considers each register-register path



99

FPGA Timing Analysis - Constraints

- ▶ The constraints file specifies timing using the TIMESPEC directive

```
#TIMESPEC <name> = FROM : <source> : TO : <dest> : <time>;
```

- ▶ In the "s3board.v" file - using predefined groups

```
# Time specifications for 50MHz clock
```

```
#
```

```
TIMESPEC TS01 = FROM : FFS : TO : FFS : 20 ns;
```

```
#TIMESPEC TS02 = FROM : RAMS : TO : FFS : 20 ns;
```

```
#TIMESPEC TS03 = FROM : FFS : TO : RAMS : 20 ns;
```

```
#TIMESPEC TS04 = FROM : RAMS : TO : RAMS : 20 ns;
```

```
TIMESPEC TS05 = FROM : FFS : TO : PADS : 20 ns;
```


```
TIMESPEC TS06 = FROM : PADS : TO : FFS : 20 ns;
```

```
#TIMESPEC TS07 = FROM : PADS : TO : RAMS : 20 ns;
```

```
#TIMESPEC TS08 = FROM : RAMS : TO : PADS : 20 ns;
```


Synchronizers

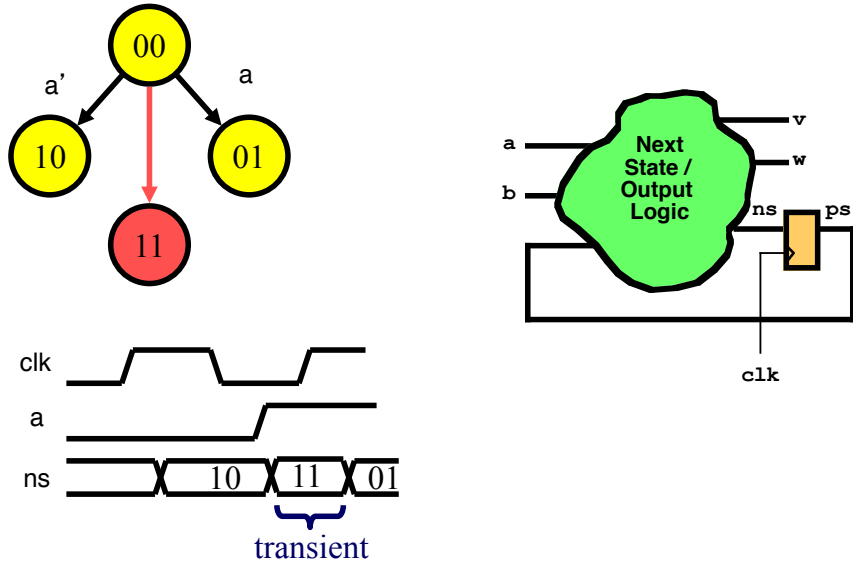- ▶ **Problem: what happens when FSM input changes at a “bad time”?**



Adding Synchronizers

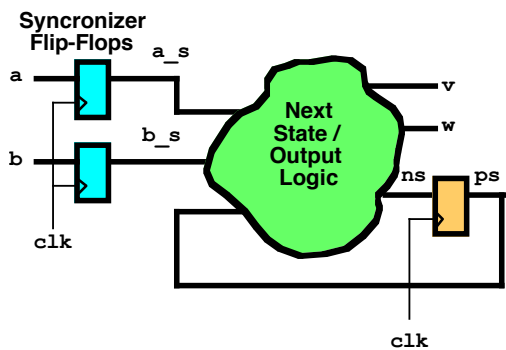- ▶ **Add a D Flip-Flop on each asynchronous input to control when it changes**
- ▶ **Synchronize each input only once**




```

reg a_s, b_s;

always @(posedge clk)
begin
    a_s <= a;
    b_s <= b;
end
    
```

Synchronizing Complete Systems

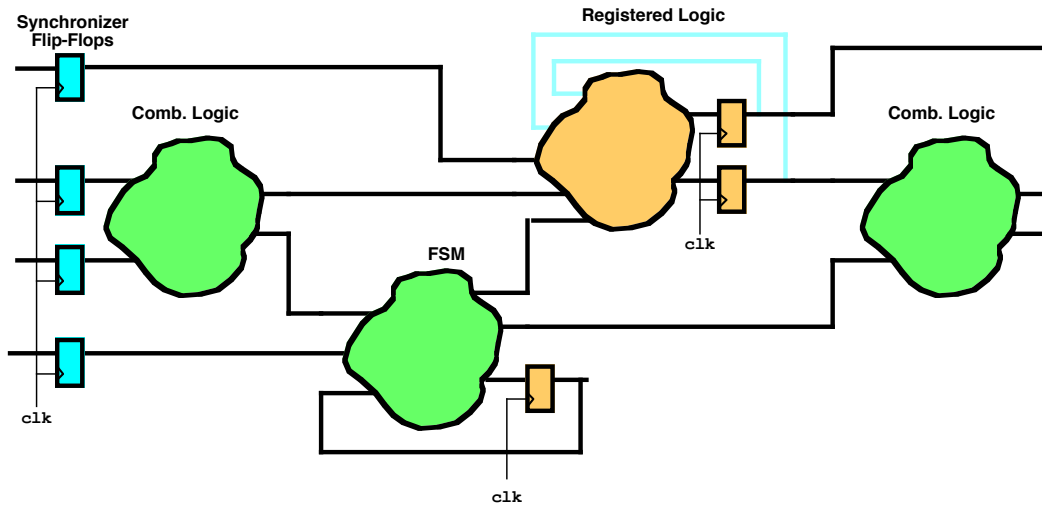


CG 4.4: Synchronize all asynchronous Inputs

CG 4.7: If possible, use a single clock.

Dealing with Multiple Clocks

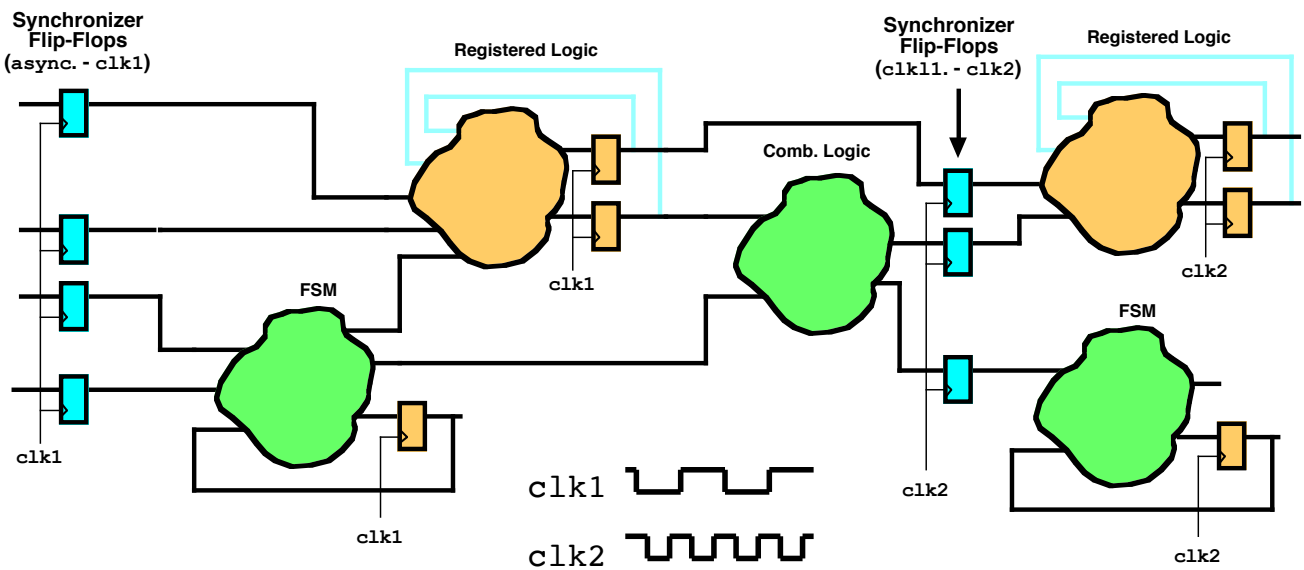► Synchronize signals between clock domains




Behavioral Modeling - Motivation

- ▶ An important tool for getting designs right!
 - ▶ Before programming FPGA (save time)
 - ▶ Before ASIC fab (save \$\$\$\$)
- ▶ In this case, think of behavior rather than hardware


Verilog and Event-Driven Simulation

 - ▶ Key idea: model circuit operation as sequence of **events** that take place at specific **times**
 - ▶ Input events - when input changes
 - ▶ Output events - response to input events (only generated when output **changes**)




Event-Driven Simulation

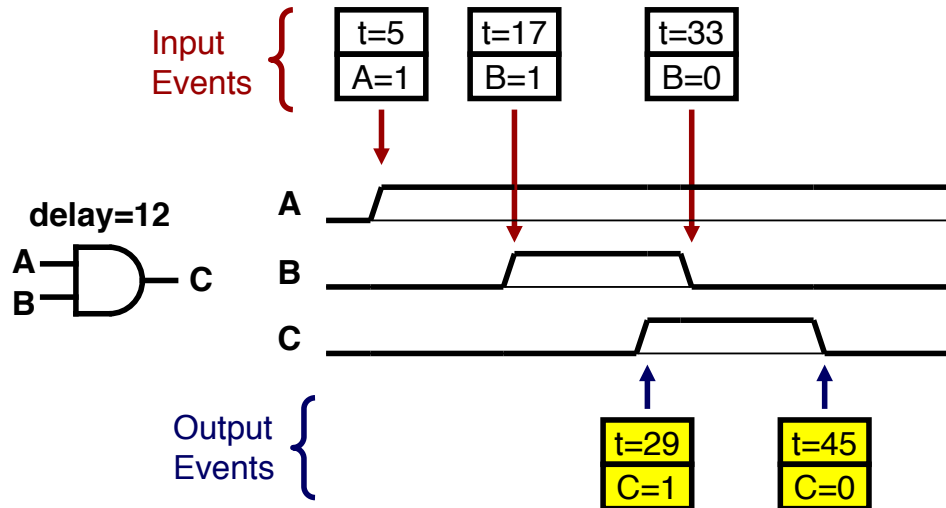- ▶ **Example: Modeling and AND Gate**
 - ▶ Input events: changes on A, B input net
 - ▶ Output events: changes on C output net after delay



Event-Driven Simulation

 - ▶ Output events from AND = input events for OR
- ▶ Simulation time “jumps” from event to event



Notes about Event-Driven Simulation

- ▶ Why use event-driven simulation? Because it's **fast**
 - ▶ Only model when signals change
 - ▶ Loss of accuracy: assumes ideal logical behavior
- ▶ What are the alternatives?
 - ▶ Circuit simulation (e.g. PSpice)
 - Numerical model of continuous behavior
 - More accurate, but slower
 - ▶ Cycle-Level Compiled code simulation
 - Model behavior in each clock cycle
 - Faster, but doesn't model delay

Event-Driven Simulation (cont'd)

- ▶ Processing Events - Data Structures
 - ▶ Event - specifies
 - **time** event will occur
 - **net** where signal will change
 - **new** value of net
 - ▶ **Event Queue** - data structure that sorts events by time
 - front of queue - earliest event
 - back of queue - latest event
- also called a **timing wheel**

Event-Driven Simulation - Algorithm

▶ Processing Events - Simulation Algorithm

```
initialization: set all nets & regs to 'x'
while (event queue not empty) {
  current_event = "earliest" event in queue;
  current_time = current_event.time;
  current_event.net.value = current_event.value;
  for (each module input connected to net) {
    evaluate(module)
    if output of module changes {
      create new event to represent output change
      add new event to queue
    }
  }
}
```

Representing Time in Verilog

- ▶ Verilog uses “dimensionless” time units
- ▶ Mapping time units to “real” time: ``timescale`

```
`timescale <time_unit> / <time_precision>
```

Time Units
of # Delay Values

Minimum step time
used by simulator

▶ Examples

```
`timescale 1ns / 1ps  
`timescale 10ns / 100ps
```


- ▶ Each module can have a different timescale (but this is not necessarily a good idea!)

Delays in Event-Driven Simulation

- ▶ Two kinds of delays supported:
 - ▶ Inertial delays - reflects limited response time in real gates
 - ▶ Transport delays - try to model delay through a wire


Inertial Delays

- ▶ What happens here?

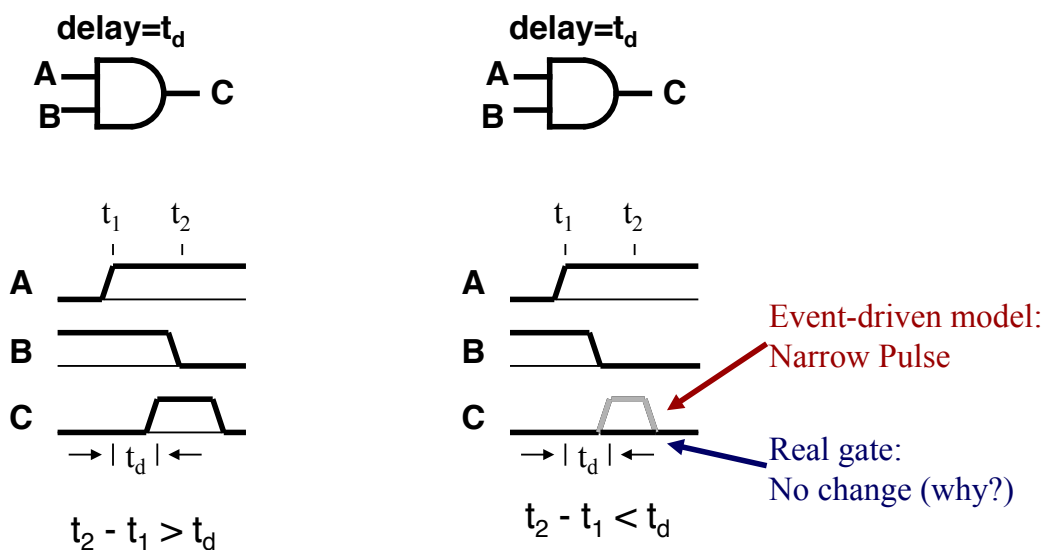


Inertial Delays in Event-Driven Simulators

 - ▶ Each signal change is scheduled in event queue
- ▶ When scheduling, compare to most recent change to calculate “pulse width”
 - ▶ If (pulse_width < prop_delay) deschedule both events



Transport Delays

- ▶ What happens here?

 

Modeling Delays in Verilog


▶ Delays in Structural Verilog

- ▶ Gate primitives: inertial delays `and #5 g1(o1, a, b);`
- ▶ Net delays (transport) `wire #5 w1;`
- ▶ More complex modules: `specify`

▶ Delays in Behavioral Verilog

- ▶ `assign` statements `assign #10 a = x & y;`
- ▶ `always` & `initial` blocks
 - blocking delay `#10 a = x + y;`
 - interassignment delay `a = #10 x + y;`

Structural Delay - Gate Primitives

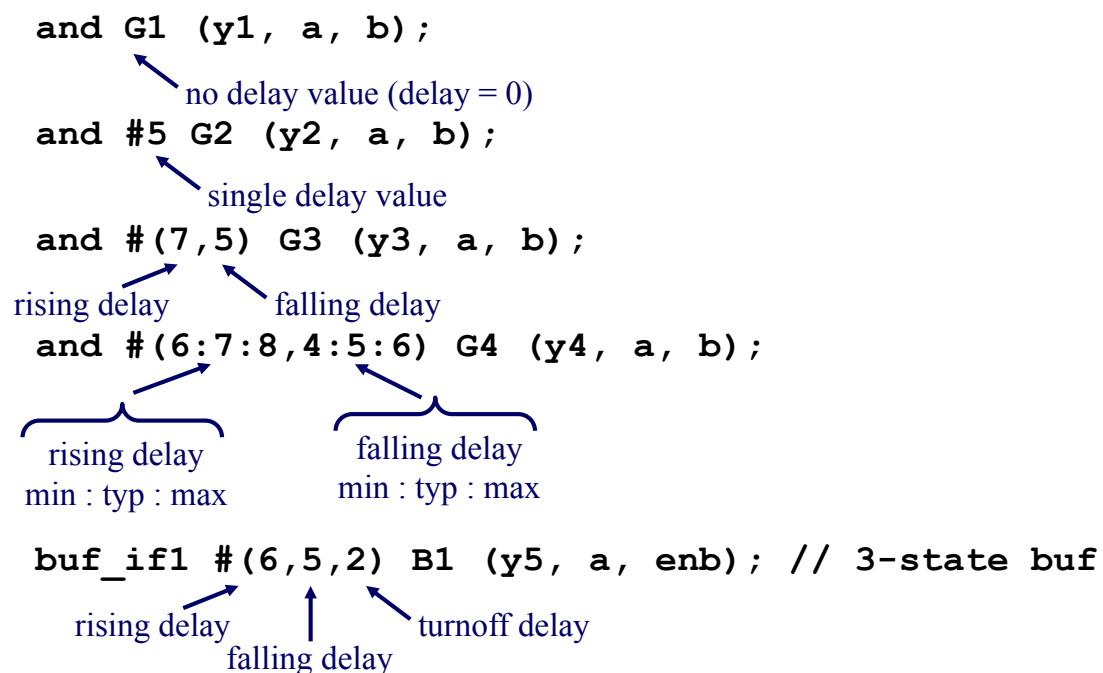

Delay in assign statements

- ▶ **Delay specified as in structural specifications**

```
assign #5 y1 = a & b;  
assign (#4,#5,$6) y2 = a & b;
```

- ▶ **Specifies inertial delay**

Delays in Behavioral Verilog

- ▶ **“Parallel” statements for procedural modeling**

- ▶ **always** - for repeated activity

```
always @(sensitivity list) sequential_statement
```

OR

```
always sequential_statement
```

Event control statement



- ▶ **initial** - for one-time activity which starts in simulation


```
initial sequential_statement
```

- ▶ **Combine with delay operators to create complex timing behavior**

initial statements

- ▶ Specify code to be executed on simulation startup
`initial sequential_statement`
- ▶ Not supported in synthesis - tell synthesis to ignore using synthesis directives (“pragmas”)
- ▶ Very useful in testbenches!
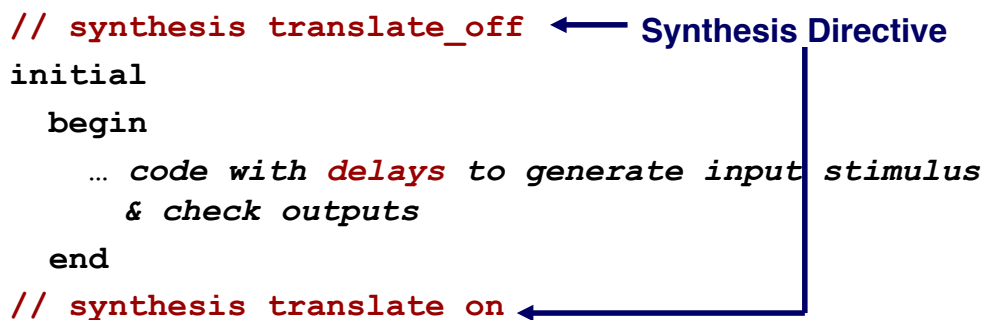
```
// synthesis translate_off ← Synthesis Directive
initial
begin
    ... code with delays to generate input stimulus
    & check outputs
end
// synthesis translate_on ←
```



Delays in Behavioral Verilog - Blocking Delay

- ▶ Delay control statement -
`#n sequential_statement`
 - ▶ Simulation effect: suspends simulation for n time units before simulating following statement

- ▶ Example: clock generator

```
always
begin
    clk = 0;
    #50 clk = 1;
    #50 ; ← null statement
end
(suspends simulation 50 time units)
```



Delays in Behavioral Verilog - Interassignment Delay

- ▶ **Key idea: unlike blocking delay, RHS is evaluated before delay**
- ▶ **With blocking assignments:**
`a = #5 b + c;` ← `b + c` evaluated; change in `a` scheduled
`d = a;` ← delayed until 5 time units elapse
- ▶ **With nonblocking assignments:**
`a <= #5 b + c;` ← `b + c` evaluated; change in `a` scheduled
`d = a;` ← executes immediately; gets OLD value of `a`!

Simulation Time in Verilog: # and `timescale

- ▶ **`timescale controls simulation time**
``timescale time_unit time_precision`

``timescale 1ns 100ps`
- ▶ **# operator specifies delay in terms of time units**
``timescale 1ns 100ps`
`#5 // delays 5*1ns = 5ns;`
`// rounds times to 100ps`

``timescale 4ns 1ns`
`#3 // delays 3*4ns = 12ns`
`// rounds times to 1ns`

What happens when no delays are specified?

- ▶ Each output event has a “delta” delay
- ▶ Events processed in order of scheduling

Verilog functions

- ▶ **Function Declaration:**
`function [range_or_type] fname;
 input_declarations
 statement
endfunction`
- ▶ **Return value: function body must assign:**
`fname = expression;`
- ▶ **Function call:** `fname (expression,...)`

Verilog Functions (cont'd)

- ▶ **Function characteristics:**
 - ▶ returns a single value (default: 1 bit)
 - ▶ can have multiple input arguments (must have at least one)
 - ▶ can access signals in enclosing module
 - ▶ can call other functions, but not tasks
 - ▶ cannot call itself (no recursion)
 - ▶ executes in zero simulation time (no timing ops allowed)
- ▶ **Synthesized as combinational logic (if proper subset is used)**

Verilog Functions (cont'd)

- ▶ **Function examples:**

```
function calc_parity;
input [31:0] val;
begin
    calc_parity = ^val;
end
endfunction

function [15:0] average;
input [15:0] a, b, c, d;
begin
    average = (a + b + c + d) >> 2;
end
endfunction;
```


Verilog Tasks

- ▶ Similar to procedures in VHDL, Pascal
- ▶ Multiple `input`, `output`, and `inout` arguments
- ▶ No explicit return value (use output arguments instead)
- ▶ No recursion allowed
- ▶ Can "enable" (call) other tasks and functions
- ▶ May contain delay, event, and timing control statements (but not in synthesis)

Verilog Tasks (cont'd)

▶ **Task example:**

```
task ReverseByte;
  input [7:0] a;
  output [7:0] ra;
  integer j;
  begin
    for (j = 7; j >=0; j=j-1)
      ra[j] = a[7-j];
    end
  end
endtask

// Adapted from "Verilog HDL Synthesis: A Practical
// Primer", by J. Bhasker
```

System Tasks and Functions

- ▶ **Tasks and functions defined for simulator control**
 - ▶ All named starting with "\$" (e.g., \$monitor)
 - ▶ Standard - same for every simulator (almost)
- ▶ **See Verilog Quick Reference Card, Section 8 for full list of system tasks**

- ▶ **Example system task: \$display**

```
$display("format-string", expr1, ..., exprn);  
    format-string - regular ASCII mixed with formatting characters  
        %d - decimal, %b - binary, %h - hex, %t - time, etc.  
    other arguments: any expression, including wires and regs  
$display("Error at time %t: value is %h, expected %h",  
        $time, actual_value, expected_value);
```

Some useful System Tasks

- ▶ **\$time** - return current simulation time
- ▶ **\$monitor** - print message when values change
 \$monitor("cs=%b, ns=%b", cs, ns)
- ▶ **Simulation control tasks**
 - ▶ \$stop - interrupt simulation
 - ▶ \$finish - terminate simulation
- ▶ **Extensive file I/O also available**

Verification

- ▶ **Goal of verification:**
 - ▶ Demonstrate **functional correctness** of a design
 - ▶ Attempt to find design errors
 - ▶ Attempt to show that design implements specification
- ▶ **Importance of Verification**
 - ▶ Costs of design errors can be high (think “Pentium Floating-Point Error” ~ \$300M!)
 - ▶ According to [1], verification consumes about 70% of design effort

[1] J. Bergeron, *Writing Testbenches: Functional Verification of HDL Models* Kluwer Academic Publishers, 2000.


Verification - Reconvergence Model

- ▶ Verification checks a “transformation” for correctness
 - ▶ RTL Design and Coding
 - ▶ Synthesis
 - ▶ Physical Design
- ▶ **Reconvergence Model:**



Verification ≠ Testing

 - ▶ Verification identifies **design errors**
 - ▶ Does the design correctly implement the specification?
 - ▶ Does it perform calculations correctly?
 - ▶ Performed **before** manufacturing
- ▶ Testing identifies **manufacturing faults**
 - ▶ Does each chip function properly?
 - ▶ Applied **after** manufacturing




Verification of RTL Design

- ▶ The Idea:




- ▶ How it Really Works:

 

Redundancy in Verification

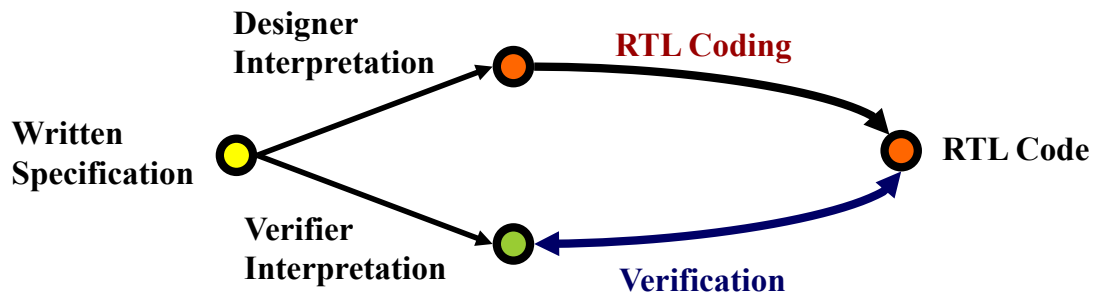- ▶ Use separate individuals for design, verification



Verification Tools

- ▶ Simulators and Testbenches
- ▶ Hardware Prototyping
- ▶ Other Tools (we won't use these)
 - ▶ Linting Tools
 - ▶ Code Coverage Tools
 - ▶ Formal Verification Tools
 - ▶ Version Control
 - ▶ Issue Tracking


Simulators

- ▶ **Allow testing of system response to stimulus**
 - ▶ Event-driven - including delay models
 - ▶ Cycle-level - one evaluation per clock cycle
- ▶ **Simulation Tools**
 - ▶ Waveform viewer
 - ▶ **Testbenches** - provide stimulus, check response
 - ▶ 3rd party models - simulate existing designs
 - Full models
 - Bus-functional models
- ▶ **Limitations of simulation**
 - ▶ Can't be exhaustive for non-trivial designs
 - ▶ Performance bottleneck


Testbenches

- ▶ A **testbench** (test fixture) is HDL code to **verify** a module
 - ▶ Apply input vectors to module inputs
 - ▶ Check module outputs
 - ▶ Report errors to user
- ▶ **Why use a testbench instead of Verilogger TDE?**
 - ▶ Portability - testbench will work on any HDL simulator
 - ▶ Automatic checking - don't have to interpret waveform
 - ▶ Expressability - can use the full semantics of HDL to:
 - generate input vectors (possibly from input file)
 - **check** output vectors
 - control simulation


Coding Testbenches in Verilog HDL

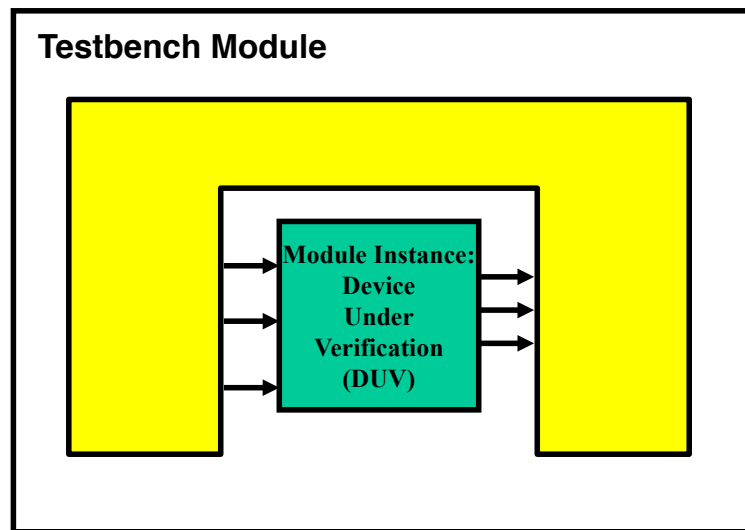


Testbench Approaches - Visual Inspection

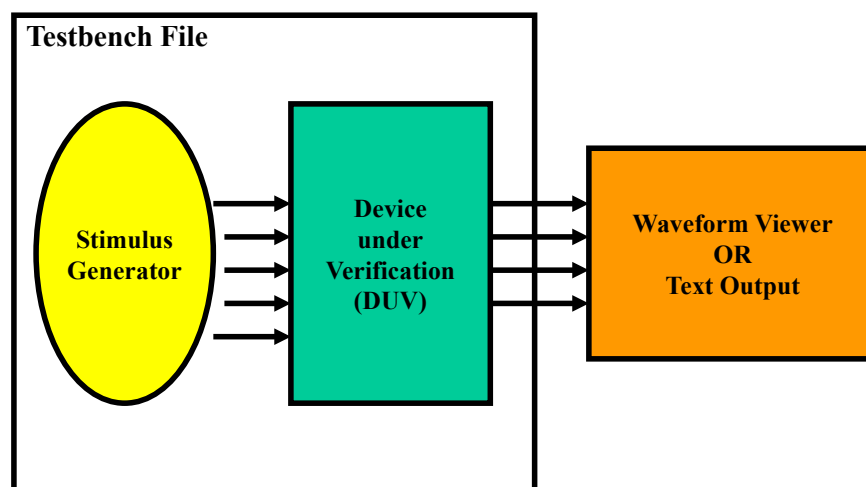

Testbench Approaches - Output Comparison

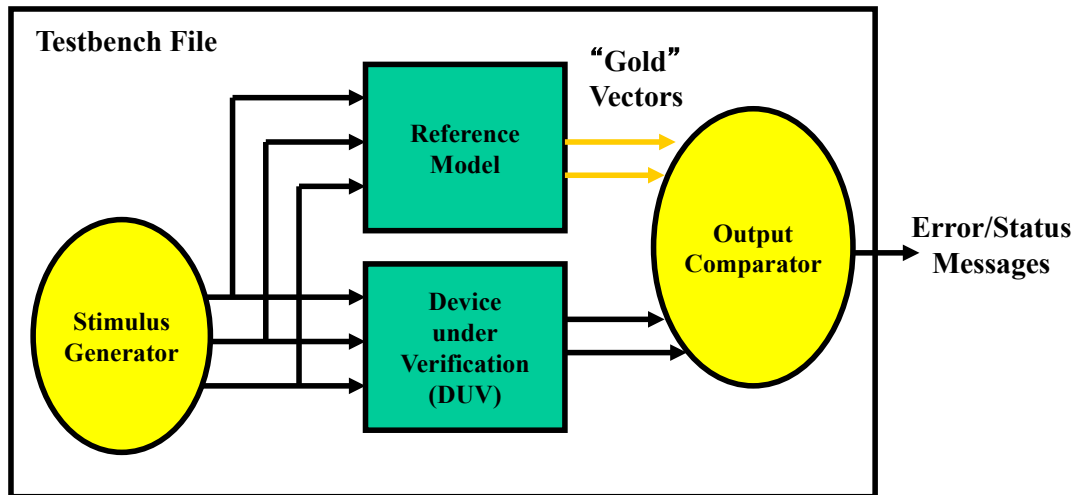

Testbench Approaches - Self-Checking

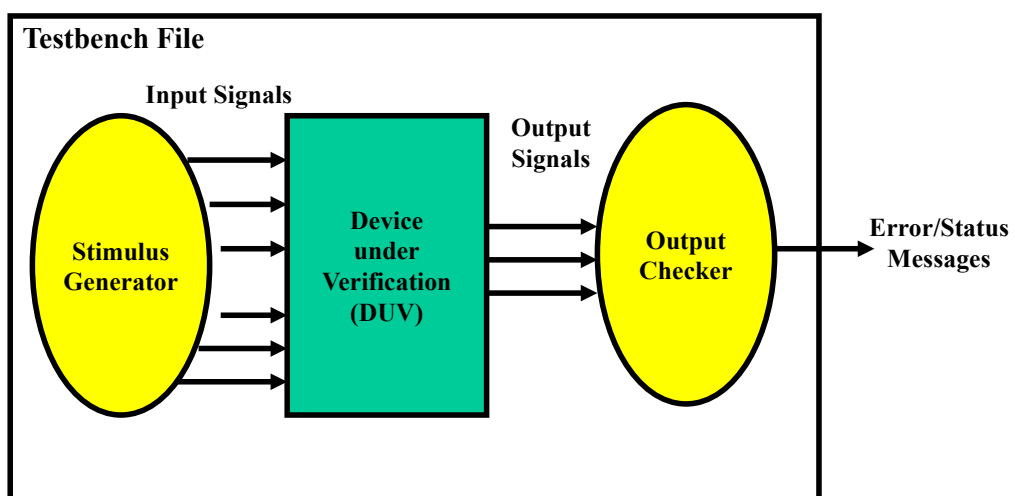

Comparing Approaches

- ▶ **Visual inspection**
 - ▶ Only practical for small designs
 - ▶ Automatic support: Verilogger timing diagram editor
- ▶ **Output comparison**
 - ▶ Effective when a good reference model is available
 - ▶ Used by ASIC foundries - “Gold” vectors are contractual specification of a “functional” chip
- ▶ **Self-checking (our focus)**
 - ▶ Most difficult to code
 - ▶ Mandatory for large designs

Coding Testbenches

- ▶ Use **simulation** features of HDL
 - ▶ `initial` blocks
 - ▶ Functions & tasks
 - ▶ System Tasks

Verilog Testbench Design

- ▶ **General approach:**
 - ▶ Use `initial` block to apply vectors
 - ▶ Use `#` delay operator to sequence input changes in time
Use `@` operator to synchronize with clock
 - ▶ Use `$display` to show output, print messages
- ▶ **Common variations**
 - ▶ Write a task (procedure) to do common checking
 - ▶ Use a separate `always` block to generate the clock

Testbench Example - Comb. Logic

- ▶ **Develop a testbench for a comparator module**

```
module compare (a, b, aeqb, agtb, altb);  
    input [7:0] a, b;  
    output aeqb, agtb, altb;  
  
    assign aeqb = (a == b);  
  
    assign agtb = (a > b);  
  
    assign altb = (a < b);  
endmodule
```

- ▶ **Do a simple test - no checking (yet)**

Testbench for Compare Module

```
module compare_bench;
  reg [7:0] a, b;
  wire aeqb, agtb, altb;

  compare DUV(a,b,aeqb,agtb,altb);

  initial begin
    a = 0;
    b = 0;
    #10
    a = 1;
    b = 0;
    #10
    a = 255;
    b = 5;
    #10
    b = 255;
    #10
    a = 127;
    #10
    $stop();
  end // initial
endmodule
```

Testbench Example - Sequential Logic

► **Develop a testbench for this BCD counter:**

```
module bcdcounter(clk, reset, enb, Q, carry);
  input clk, reset, enb;
  output [3:0] Q;
  output carry;

  reg [3:0] Q; // a signal that is assigned a value

  assign carry = (Q == 9) & enb;

  always @(posedge clk)
  begin
    if (reset) Q <= 4'd0;
    else if (enb)
      begin
        if (carry) Q <= 0;
        else Q <= Q + 1;
      end
  end
endmodule
```

BCD Counter Testbench - Design Ideas

- ▶ Use a separate `always` statement to drive clock (must set at beginning of `initial` block)
- ▶ Write a task to check values
- ▶ Use `$display` system task for error messages

Testbench for BCD Counter

```
module bcdcounter_bench;

    // signals for connecting the counter
    reg      clk;
    reg      reset;
    reg      enb;
    wire [3:0] Q;
    wire      carry;

    // testbench variables;
    integer  i;

    // counter instance
    bcdcounter DUT(.clk(clk), .reset(reset), .enb(enb),
                  .Q(Q), .carry(carry));
endmodule
```

Testbench for BCD Counter (cont'd)

```
task check;
  input [3:0] Q, check_Q;
  input carry, check_carry;

  begin
    if (Q != check_Q)
      $display("Error at time %t: Expected Q=%d, Actual Q=%d",
        $time, check_Q, Q);
    if (carry != check_carry)
      $display("Error at time %t: Expected carry=%d, Actual carry=%d",
        $time, check_carry, carry);
  end
endtask

// note clock drives both counter and bench
always
  begin
    clk = 0;
    #5 clk = 1;
    #5 ;
  end
```

Testbench for BCD Counter (cont'd)

```
initial begin
  reset = 0;
  enb = 0;
  @(posedge clk);
  // do a reset and check that it worked
  reset = 1;
  @(posedge clk);
  check(Q,0,carry,0);

  // now try counting a few cycles
  #1 reset = 0;
  #1 enb = 1;
  for (i=0; i<9; i=i+1)
    begin
      @(posedge clk);
      check(Q,i,carry,0); // exhaustively test counter
    end
end
```

Testbench for BCD Counter (cont'd)

```
// now check the carry count should be 9!
@(posedge clk);
check(Q,9,carry,1);
// now check the rollover
@(posedge clk);
check(Q,0,carry,0);
// intentional error - count !=2, carry != 1
@(posedge clk)
check(Q,2,carry,0);
check(Q,1,carry,1);
repeat (7) @(posedge clk);
#1 check(Q,9,carry,1);
#5 enb = 0;
#2 check(Q,9,carry,0);
repeat (3) @(posedge clk);
$stop(); // all done!
end // initial
endmodule
```

Testbench Design

- ▶ **How do we verify designs that are too large for exhaustive simulation?**
 - ▶ **Identify key features**
 - How do we exercise?
 - What is correct response?
 - ▶ **Identify “Corner cases”**
 - Initial conditions
 - “Boundaries” between modes of operation
 - ▶ **Ensure code coverage**
 - Does testbench exercise all of the Verilog code?
 - Commercial coverage tools help this process
 - ▶ **Use random inputs to test unanticipated cases**

Verification of Large Designs


- ▶ Create a **verification plan** which specifies
 - ▶ Features necessary for first-time success
 - Prioritization of features - essential vs. optional
 - Which features should be exercised
 - What the response should be
 - ▶ Testcases to exercise features
 - ▶ Process for reporting and fixing bugs
- ▶ Implement testbenches for each testcase
- ▶ Report bugs & fix
- ▶ Big question: when are you done?

More about Testbenches

- ▶ Testbenches are essential in large designs
 - ▶ Design team may include hundreds of people, who work on different subsystems
 - ▶ Testbenches allow semi-automatic checking when different subsystems are changed (**regression**)
 - ▶ Chip design groups do this with "**simulation farms**"




Testbenches in Hierarchical Design

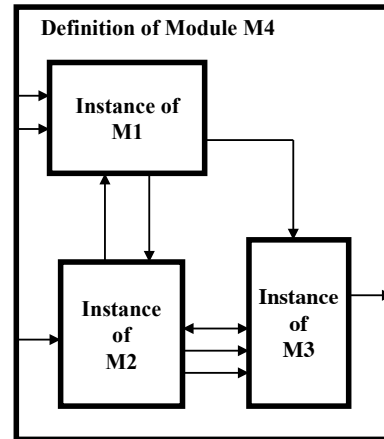- ▶ **Example Hierarchy**
 - ▶ Module M4 - Top-level module
 - ▶ Modules M1, M2, M3 - used as instances in M4
- ▶ **Create testbenches for all modules M1, M2, M3, M4**
- ▶ **What if we change M2?**
 - ▶ First run M2 testbench
 - ▶ Next, run M4 testbench



Functional Verification Approaches

- ▶ **Black box**
 - ▶ Verify using module I/O ports only
 - ▶ No knowledge of implementation
 - ▶ No access to internals
- ▶ **White box**
 - ▶ Verify using module I/O ports and internals
 - ▶ Full knowledge of implementation
 - ▶ Full access to internals during simulation
- ▶ **Gray box**
 - ▶ Verify using module I/O ports only
 - ▶ Full knowledge of implementation
 - ▶ No access to internals during simulation

   

Linting Tools

- ▶ **Key idea: check code for potential problems that are legal HDL but not desirable, e.g.:**
 - ▶ Latch inferences
 - ▶ Wire size mismatches
 - ▶ Implicit declarations
- ▶ **Types of Linting Tools**
 - ▶ Commercial tools
 - ▶ Code reviews - peer review
- ▶ **Limitations**
 - ▶ Sometimes report non-problems
 - ▶ Can't look beyond syntax - "spell checker" analogy

Code Coverage Tools

- ▶ **Key idea: check that all code is simulated**
 - ▶ Check that all lines of code are exercised in simulation
 - ▶ Check that all paths through conditionals are exercised
- ▶ **Coverage tool function**
 - ▶ Insert reporting code into HDL model
 - ▶ Summarize coverage & report to user
 - ▶ Key metric % coverage
- ▶ **Limitations**
 - ▶ 100% coverage difficult to accomplish
 - ▶ No guarantee of correctness

Other Verification Tools

- ▶ **Verification languages (e.g. e, Vera)**
 - ▶ Used to specify and generate testbenches
 - ▶ Abstraction used to increase productivity
 - ▶ Focus on **constrained random** stimulus
- ▶ **Revision control - used as in software engineering**
- ▶ **Formal Verification**
 - ▶ Equivalence checking - prove that input, output are equivalent
 - ▶ Model checking - Prove assertions concerning design properties, e.g.
 - Reachability of states
 - Deadlock avoidance
 - Completion of transaction in an interface